

## ECE 574 – VLSI System Design

Homework n°2

Amine Gaizi

[gaizia@oregonstate.edu](mailto:gaizia@oregonstate.edu)

Student ID: 934-044-900

1. The Verilog code:

```
//Module Declaration: input and outputs
module alu(
    input[7:0] in_a,    //input a
    input [7:0] in_b,    //input b
    input [3:0] opcode,    //opcode input
    output reg [7:0] alu_out, //alu output
    output reg alu_zero, //logic '1' when alu_output [7:0] is all zeros
    output reg alu_carry //indicates a carry out from AKY
);

//Declaration of the opcodes value in Hexadecimal
parameter c_add = 4'h1;
parameter c_sub = 4'h2;
parameter c_inc = 4'h3;
parameter c_dec = 4'h4;
parameter c_or = 4'h5;
parameter c_and = 4'h6;
parameter c_xor = 4'h7;
parameter c_shr = 4'h8;
parameter c_shl = 4'h9;
parameter c_onescomp = 4'hA;
parameter c_twoscomp = 4'hB;

always_comb begin //a
    unique case(opcode) //unique modifier because only one option can match
        c_add: {alu_carry, alu_out} = in_a + in_b; //Arithmetic addition
        c_sub: {alu_carry, alu_out} = in_a - in_b; //Arithmetic subtraction
        c_inc: {alu_carry, alu_out} = in_a + 1; //Arithmetic incrementation
        c_dec: {alu_carry, alu_out} = in_a - 1; //Arithmetic decrementation
        c_or:
            begin
                alu_out = in_a | in_b; //Logic OR operation
                alu_carry = 0; //Reset carry
            end

        c_and:
            begin
                alu_out = in_a & in_b; //Logic AND operation
                alu_carry = 0; //Reset carry
            end

        c_xor:
            begin
                alu_out = in_a ^ in_b; //Logic XOR operation
                alu_carry = 0; //Reset carry
            end
    endcase
end
```


```


begin
    alu_out = in_a ^ in_b; //Logic XOR operation
    alu_carry = 0; //Reset carry
end

c_shr:
begin
    alu_out = in_a>>1; //Right shifting
    alu_carry = 0; //Reset carry
end
c_shl: {alu_carry, alu_out} = 1<<in_a; //Left shifting
c_onescomp: alu_out = ~in_a;
c_twoscomp:
begin
    alu_out = ~in_a; //Invert
    {alu_carry, alu_out} = alu_out+1; //Add 1
end
default: {alu_carry, alu_out} = 9'b000000000; //If no match, reset alu_out and alu_carry
endcase
alu_zero = ~| alu_out; // NOR operation so: if alu_out = 0, alu_zero=1
end
endmodule

```

## 2. Schematic of the designed ALU:

 

 3. Waveform of the code working correctlya. RTL levelb. Gate levelc. Test code

```
#undefined start
force in_a 8'h00
force in_b 8'h00
force opcode 4'b0000
```

```
run 20

#add 8+2 = 0xA
force in_a 8'h08
force in_b 8'h02
force opcode 4'b0001
run 20

#add test carry
# 0xE1 + 0x1F = 0x00 and Carry=1
force in_a 8'hE1
force in_b 8'h1F
force opcode 4'b0001
run 20

#subtract 0x0E - 0x07 = 0x07
force in_a 8'h0E
force in_b 8'h07
force opcode 4'b0010
run 20

#increment 0x0F + 0x01 = 0x10
force in_a 8'h0F
force in_b 8'hXX
force opcode 4'b0011
run 20

#decrement expected result: 0x05
force in_a 8'h06
force in_b 8'hXX
force opcode 4'b0100
run 20

#logic or, 0b00001001 | 0b00001111 = 0b00001111
force in_a 8'b00001001
force in_b 8'b00001111
force opcode 4'b0101
run 20

#logic and
force in_a 8'b11111101
force in_b 8'b10101010
force opcode 4'b0110
run 20

#logic xor
force in_a 8'b10101111
force in_b 8'b01010001
force opcode 4'b0111
run 20

#wrong OP code for XOR -> goes to default
force in_a 8'b10101111
```

```
force in_b 8'b01010001
force opcode 4'b1111
run 20
```

```
#logic shift right
force in_a 8'b10000000
force in_b 8'hXX
force opcode 4'b1000
run 20
```

```
#logic shift left
force in_a 8'b11111111
force in_b 8'hXX
force opcode 4'b1001
run 20
```

```
#logic ones compe
force in_a 8'h08
force in_b 8'hXX
force opcode 4'b1001
run 20
```

```
#logic twos comp
force in_a 8'h4D
force in_b 8'hXX
force opcode 4'b1010
run 20
```

#### 4. Written answers:

##### a. Total area used by the ALU

The total area use by the ALU is: 1814.079795  $\mu m^2$ .

##### b. Number of different cells utilized

Report hierarchy displays:

AND2X1	saed90nm_typ
AND3X1	saed90nm_typ
AO21X1	saed90nm_typ
AO22X1	saed90nm_typ
AO221X1	saed90nm_typ
AO222X1	saed90nm_typ
AOI222X1	saed90nm_typ
INVX0	saed90nm_typ
LATCHX1	saed90nm_typ
MUX21X1	saed90nm_typ
NAND2X0	saed90nm_typ
NAND3X0	saed90nm_typ
NAND4X0	saed90nm_typ
NOR2X0	saed90nm_typ

OR2X1	saed90nm_typ
OR4X1	saed90nm_typ
XNOR2X1	saed90nm_typ
alu_DW01_addsub_0	
FADDX1	saed90nm_typ
XOR2X1	saed90nm_typ
alu_DW01_ash_0	
AND2X1	saed90nm_typ
AO21X1	saed90nm_typ
INX0	saed90nm_typ
NAND2X0	saed90nm_typ
NAND3X0	saed90nm_typ
NOR2X0	saed90nm_typ
OR3X1	saed90nm_typ

This totals to 26 different gates utilized.

c. Number of cells:

$$\text{Gate equivalent count} = \frac{\text{Total Area}}{\text{NAND2X1 area}} = \frac{1814.079795}{5.5296} = 328,067$$

The equivalent gate count is 328 gates.

d. Hierarchical block:

The block is an adder subtractor ("alu\_DW01\_addsub"). It is implemented using a full adder block and an XOR logic gate.

e. Delay:

The maximum delay through the ALU is 2.68ns. The beginning point is "opcode[0](input port)", and the endpoint is "alu\_zero(output\_port)".